

ASSIGNMENT 4

TADIPATRI UDAY KIRAN REDDY
EE19BTECH11038

February 28, 2022

Problem 1

First we find out the V^+ using below procedure and here $\Gamma_L = \frac{R_L - z_0}{R_L + z_0}$

$$V(x) = V^+ e^{-\gamma x} (1 + \Gamma_L e^{2\gamma x}) \quad (1)$$

$$I(x) = \frac{V^+}{z_0} e^{-\gamma x} (1 - \Gamma_L e^{2\gamma x}) \quad (2)$$

$$\Rightarrow V_{in} = V_s - I(-l)r_s = V(-l) \quad (3)$$

$$\Rightarrow V_s - V^+ \frac{r_s}{z_0} e^{\gamma l} (1 - \Gamma_L e^{-2\gamma l}) = V^+ e^{\gamma l} (1 + \Gamma_L e^{-2\gamma l}) \quad (4)$$

$$\Rightarrow V^+ = V_s \frac{e^{-\gamma l}}{\frac{r_s}{z_0} (1 - \Gamma_L e^{-2\gamma l}) + (1 + \Gamma_L e^{-2\gamma l})} \quad (5)$$

We use this V^+ to compute V_0 ,

$$V_0 = V(0) = V^+ (1 + \Gamma_L) \Rightarrow V_0 = V_s \frac{(1 + \Gamma_L) e^{-\gamma l}}{\frac{r_s}{z_0} (1 - \Gamma_L e^{-2\gamma l}) + (1 + \Gamma_L e^{-2\gamma l})} \quad (6)$$

$$\Rightarrow V_0 = V_s \frac{2z_0 R_L}{(z_0^2 + R_L r_s)(e^{\gamma l} - e^{-\gamma l}) + (z_0(R_L + r_s))(e^{\gamma l} + e^{-\gamma l})} \quad (7)$$

Sanity check


As $l = 0$,

$$V_0 = V_s \frac{2z_0 R_L}{z_0(R_L + r_s)2} = V_s \frac{R_L}{r_s + R_L} \quad (8)$$

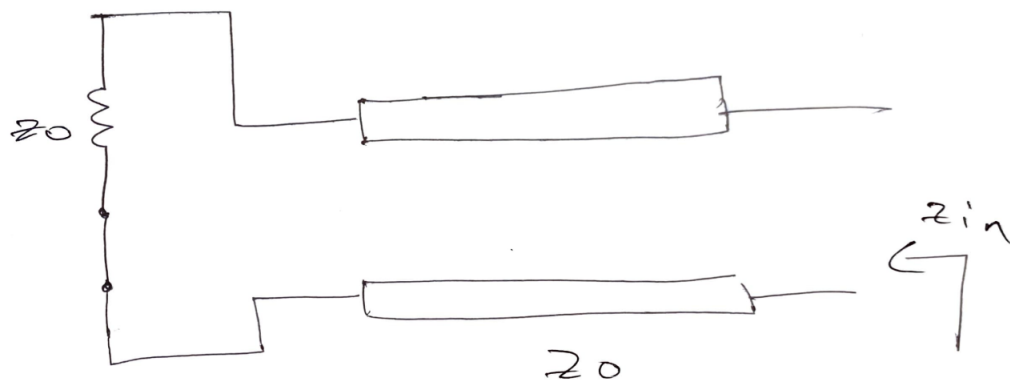Problem 2

Thevinin resistance

It is just input impedance but from load side, thus input resistance is load which means $\Gamma_L = 0$ since it is matching network.




$$Z_{th} = Z_{in}(l) = z_0 \frac{1 + \Gamma_L e^{-2\Gamma_L l}}{1 - \Gamma_L e^{-2\Gamma_L l}} \quad (9)$$

$$Z_{th} = z_0 \quad (10)$$


Thevinin voltage

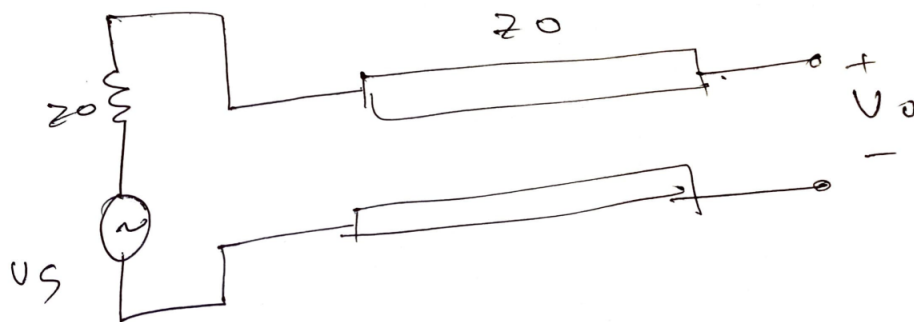As obtained from previous problem here load is open circuited.



$$V_{th} = V_0|_{R_L \rightarrow \infty} = V_s \frac{2z_0}{\left(\frac{z_0^2}{R_L} + z_0\right)(e^{\gamma l} - e^{-\gamma l}) + (z_0(1 + \frac{z_0}{R_L}))(e^{\gamma l} + e^{-\gamma l})} \Big|_{R_L \rightarrow \infty} \quad (11)$$

$$V_{th} = V_s e^{-\gamma l} \quad (12)$$

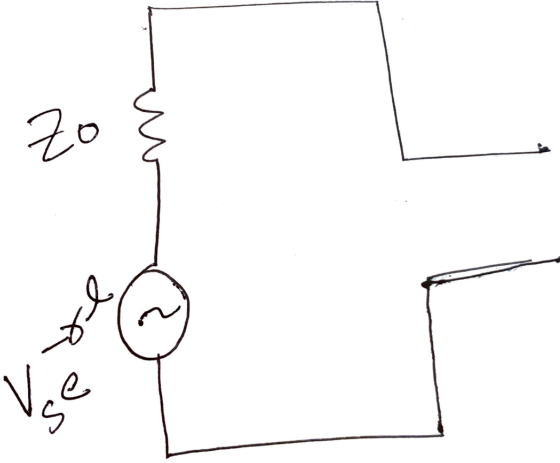

Problem 3

$$\frac{V_2}{V_1} = \frac{V(l)}{V(0)} = \frac{e^{j\beta l} + \Gamma_L e^{-j\beta l}}{1 + \Gamma_L} \quad (13)$$

Since it is open circuit, $\Gamma_L = 1$

$$V_2 = V_1(e^{j\beta l} + e^{-j\beta l})/2 \quad (14)$$

Delay can be computed using phase velocity $V_p = 1/\beta = l/t_d$

This means that delay in that transmission line is

$$t_d = \beta l = \sqrt{L_0 C_0} l = z_0 C_0 l = z_0 C_T$$

Since, $z_0 = \sqrt{\frac{L_0}{C_0}}$ and $C_T = C_0 l$