


ASSIGNMENT 7

TADIPATRI UDAY KIRAN REDDY
EE19BTECH11038

April 18, 2022

Problem 1


(a)

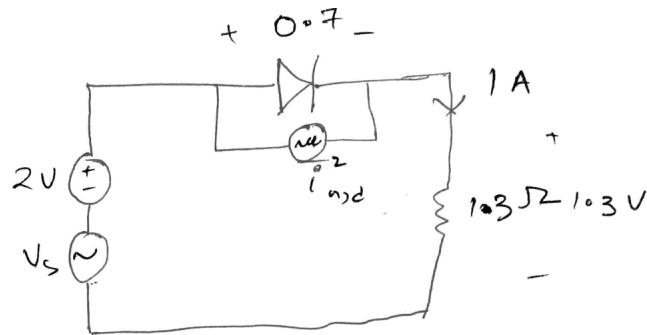

$$I_D = 1A$$

$$V_o = 1.3 + V_s$$

(b)

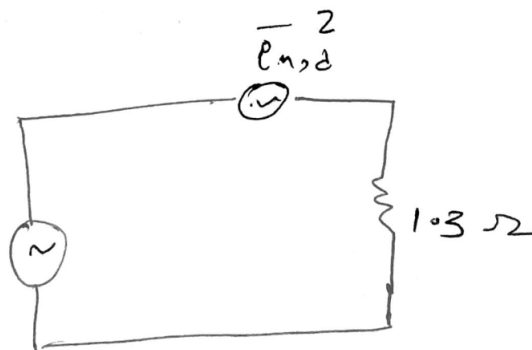

$$NoisePSD = 1.69 * 2 * 1.6 * 10^{-19} * 1$$

$$\Rightarrow NoisePSD = 5.41e - 19W/Hz$$

(c)



Here the gain is 1, any addition of resistance in series will reduce the gain. Thus there is **no resistance which can give the same gain.**

Problem 2

For the total chain,

$$F_{eff} = 1 + \frac{V_{n,in_3}^2}{(A_{p1}A_{p2}A_{p3})^2 V_{n,s}^2} + \frac{V_{n,in_2}^2}{(A_{p1}A_{p2})^2 V_{n,s}^2} + \frac{V_{n,in_1}^2}{(A_{p1})^2 V_{n,s}^2}$$

Take intermediate stage say ith stage,

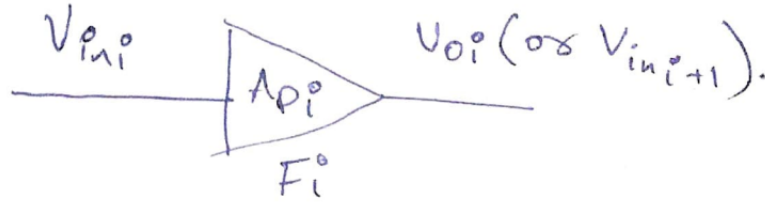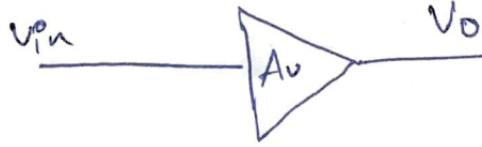

$$F_i = \frac{A_{pi}^2 V_{n,in_i}^2 + V_{n,in_{i+1}}^2}{A_{pi}^2 V_{n,in_i}^2} = 1 + \frac{V_{n,in_{i+1}}^2}{A_{pi}^2 V_{n,in_i}^2}$$

And since, $A_{pi} = \frac{V_{in_{i+1}}}{V_{in_i}}$.

$$F_{eff} = 1 + (1 - F_1)(1 - F_2)(1 - F_3) + (1 - F_1)(1 - F_2) + (1 - F_1)$$

Problem 3

We find gain from input to output and just multiply the input noise PSD with square of magnitude of gain.

(a)

$$\frac{V_o}{V_{in}} = \frac{1}{sCR + 1}$$

$$NoisePSD = AvAv^* V_n^2 \Rightarrow$$

$$NoisePSD = \frac{1}{1 + (\omega CR)^2}$$

(b)

$$\frac{V_o}{V_{in}} = \frac{1}{s^2 LC + sCR + 1}$$

$$\Rightarrow \text{NoisePSD} = \frac{V_n^2}{(1 - \omega^2 LC)^2 + (\omega CR)^2}$$

(c)

$$\frac{V_{o1}}{V_{in}} = \frac{s^2 LC_2 + 1}{s^3 RLC_1 C_2 + s^2 LC_2 + sR(C_1 + C_2) + 1}$$

$$\Rightarrow \text{NoisePSD}_1 = V_n^2 \frac{(1 - \omega^2 LC_2)^2}{(1 - \omega^2 LC_2)^2 + (\omega^3 RLC_1 C_2 - \omega R(C_1 + C_2))^2}$$


$$\frac{V_{o2}}{V_{in}} = \frac{1}{s^3 RLC_1 C_2 + s^2 LC_2 + sR(C_1 + C_2) + 1}$$

$$\Rightarrow \text{NoisePSD}_2 = V_n^2 \frac{1}{(1 - \omega^2 LC_2)^2 + (\omega^3 RLC_1 C_2 - \omega R(C_1 + C_2))^2}$$

Problem 4

(a)


Small signal model

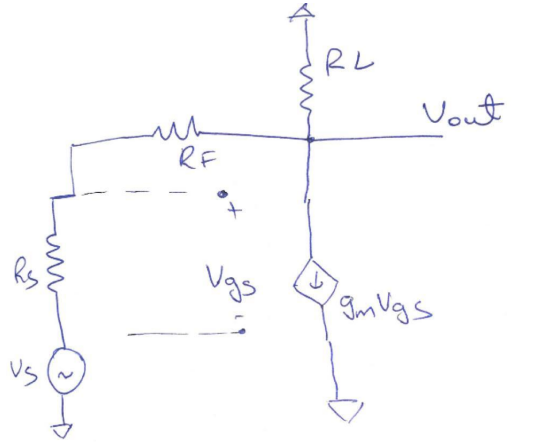


Effective gain here is $A_v = \frac{V_{out}}{V_s} = -\frac{(g_m - 1/R_F)R_L}{1 + \frac{1}{R_F}(R_L + R_s + g_m R_s R_L)}$.

Miller approximation


The following circuits are equivalent.

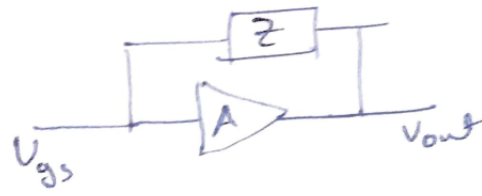

|||

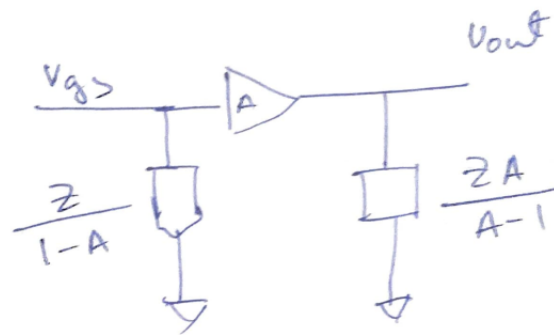

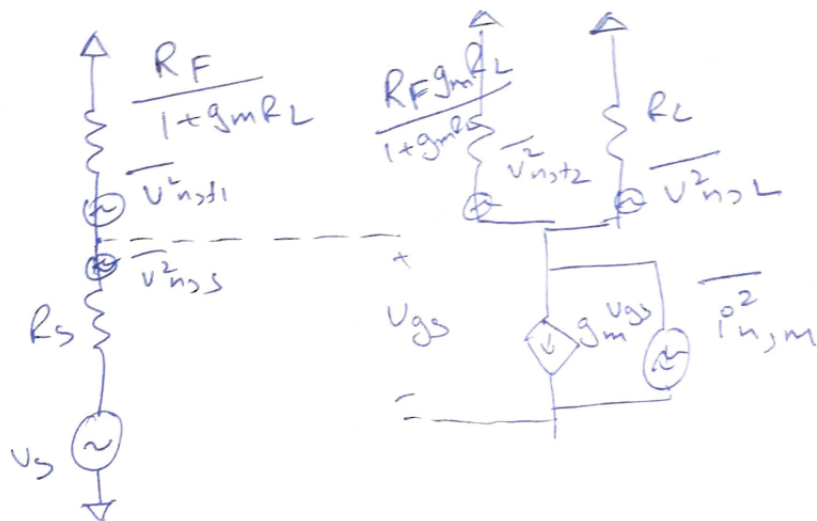
Applying miller approximation on our small signal circuit we get, here A is open loop gain which is $-g_m R_L$




$$\begin{aligned}
I/PNoise &= 4KT \left(R_s + \frac{R_F}{1 + g_m R_L} \right) \left(g_m \left(R_L \parallel \frac{g_m R_L}{1 + g_m R_L} R_F \right) \right)^2 \\
O/PNoise &= I/PNoise + 4KT r_{gm} \left(R_L \parallel \frac{g_m R_L}{1 + g_m R_L} R_F \right)^2 + 4KT \left(\frac{g_m R_L}{1 + g_m R_L} R_F \right) \\
NF &= \frac{O/PNoise}{I/PNoise} \\
\Rightarrow NF &= 1 + \frac{r}{g_m \left(R_s + \frac{R_F}{1 + g_m R_L} \right)} + \frac{\left(\frac{g_m R_L}{1 + g_m R_L} R_F \right)}{g_m^2 \left(R_s + \frac{R_F}{1 + g_m R_L} \right) \left(R_L \parallel \frac{g_m R_L}{1 + g_m R_L} R_F \right)^2} \\
R_F &\gg g_m R_L R_s \\
\Rightarrow NF &= 1 + \frac{r R_L}{R_F} + \frac{R_L}{g_m R_F}
\end{aligned}$$

(b)

Small signal model

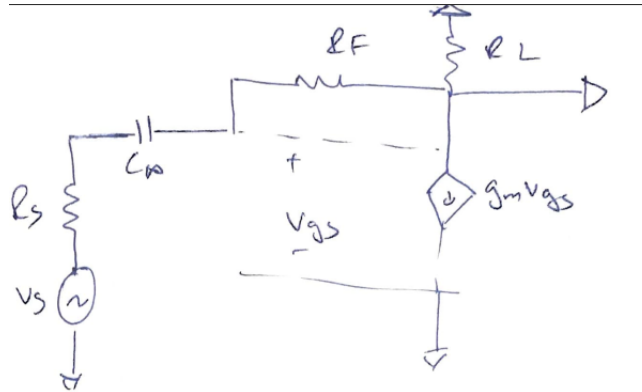

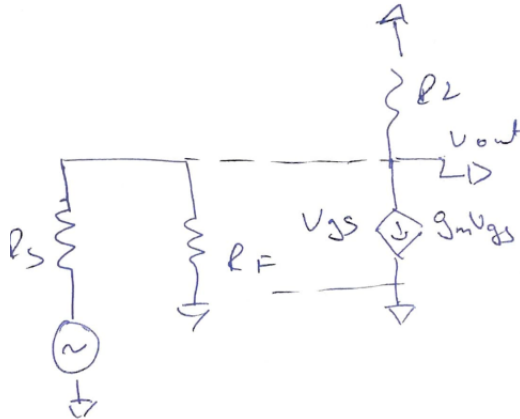The gain here is zero. Thus using miller approximation. At output only noise would appear.



$$I/P_{Noise} = 4KT(R_s + R_F)$$


$$O/P_{Noise} = 4KT(R_s + R_F) + 4KT r_{gm} R_L^2$$

$$\Rightarrow F = 1 + \frac{r_{gm} R_L^2}{R_s + R_F}$$

Problem 5

We can find Z-parameters for both the models and just equate corresponding parameters.

Model 1

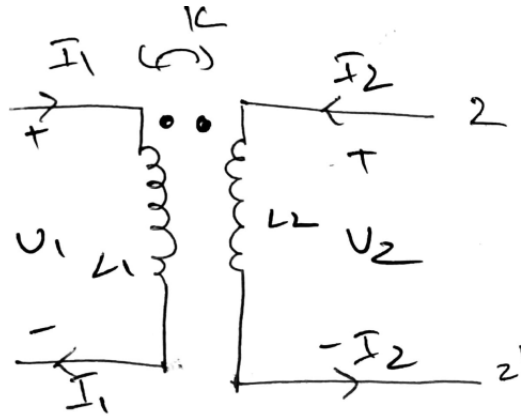


$$V_1 = sL_1 I_1 + sM I_2$$

$$V_2 = sM I_1 + sL_2 I_2$$

$$M = K\sqrt{L_1 L_2}$$

Model 2

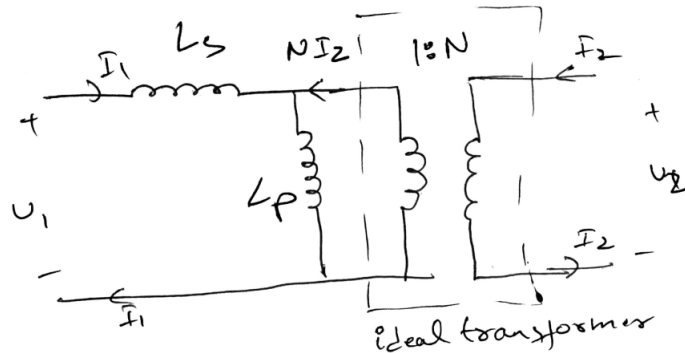

$$V_1 = s(L_s + L_p)I_1 + sNL_p I_2$$

$$V_2 = sNL_p I_1 + sN^2 L_p I_2$$

From above equations we conclude that,

$$\begin{aligned}
 L_1 &= L_s + L_p \\
 NL_p &= K\sqrt{L_1 L_2} \\
 N^2 L_p &= L_2 \\
 \Rightarrow N &= \frac{1}{K} \sqrt{\frac{L_2}{L_1}} \\
 \Rightarrow L_p &= K^2 L_1 \Rightarrow L_s = (1 - K^2) L_1
 \end{aligned}$$

Problem 6

At receiver,

$$\begin{aligned}
 NF &= SNR_{in} - SNR_{out} = 10dB \\
 SNR_{in} &= 10dB + SNR_{out} \geq 10dB \\
 \Rightarrow P_{Rx} &\geq P_{noise} + 10dB \Rightarrow P_{Tx} - P_{atten} \geq P_{noise} + 10dB \\
 \Rightarrow P_{atten} &\leq P_{Tx} - (P_{noise} + 10dB)
 \end{aligned}$$

Assuming the circuits are matched, P_{noise} would be $-173.8 + 10\log_{10}B$ which is -123.8dB. Therefore,

$$P_{atten} \leq 143.8dB$$

Maximum of 143.8dB of atmospheric attenuation is allowed.