

# ASSIGNMENT 5

TADIPATRI UDAY KIRAN REDDY  
EE19BTECH11038

March 7, 2022

## Problem 1

Effective  $Q_{eff} = Q_1 + Q_2$ , where  $Q_i = \sqrt{\frac{R_{out}}{R_{in}}} - 1$ . Since this is 2 stage low pass matching network let us take a intermediate jump of resistance  $R_i$ .

$$Q_1 = \sqrt{\frac{R_{HI}}{R_i} - 1} = \frac{\omega L_1}{R_i + R_{rs1}} = \omega C_1 R_{HI} \quad (1)$$

$$Q_2 = \sqrt{\frac{R_i}{R_{LO}} - 1} = \frac{\omega L_2}{R_{LO} + R_{rs2}} = \omega C_2 R_i \quad (2)$$

The loss in the network is because of lossy inductors which have a Q of 20.

$$\eta = \frac{P_L}{P_L + P_{rs1} + P_{rs2}} = \frac{P_L}{P_L + \frac{E_{L1} + E_{L2}}{Q}} \quad (3)$$

$$\eta = \frac{P_L}{P_L + \frac{Q_1 P_L + Q_2 P_L}{Q}} = \frac{1}{1 + \frac{Q_1 \frac{P_L}{Q} + Q_2}{Q}} \quad (4)$$

Here  $\frac{P_L}{P_2}$  is inverse of efficiency of only 2nd stage which is  $1 + \frac{Q_2}{Q}$ . Therefore,

$$\eta = \frac{1}{1 + \frac{Q_1 + Q_2 + Q_1 Q_2 / Q}{Q}} \quad (5)$$

$$\max\{\eta\} \iff \min\{Q_1 + Q_2 + Q_1 Q_2 / Q\} \quad (6)$$

$$\implies \frac{\partial}{\partial R_i} (Q_1 + Q_2 + Q_1 Q_2 / Q) = 0 \quad (7)$$

$$Q \left( \frac{\partial Q_1}{\partial R_i} + \frac{\partial Q_2}{\partial R_i} \right) + Q_1 \frac{\partial Q_2}{\partial R_i} + Q_2 \frac{\partial Q_1}{\partial R_i} = Q \left[ -\frac{R_{HI}}{2R_i^2 Q_1} + \frac{1}{2R_{LO} Q_2} \right] + Q_1 \left[ \frac{1}{2R_{LO} Q_2} \right] - Q_2 \left[ \frac{R_{HI}}{2R_i^2 Q_1} \right] = 0 \quad (8)$$

$$(9)$$

Simplifying the above equation we end up getting,


$$R_i^2 Q_1 (Q_1 + Q) = R_{HI} R_{LO} Q_2 (Q_2 + Q) \quad (10)$$

Assuming  $Q_2, Q_1 \ll Q$ ,

$$2R_i^2 Q_1 Q = R_{HI} R_{LO} Q_2 Q \quad (11)$$

$$\implies 4R_i^4 - R_{HI} R_i^3 + R_{HI}^2 R_{LO} R_i - R_{HI}^2 R_{LO}^2 = 0 \quad (12)$$
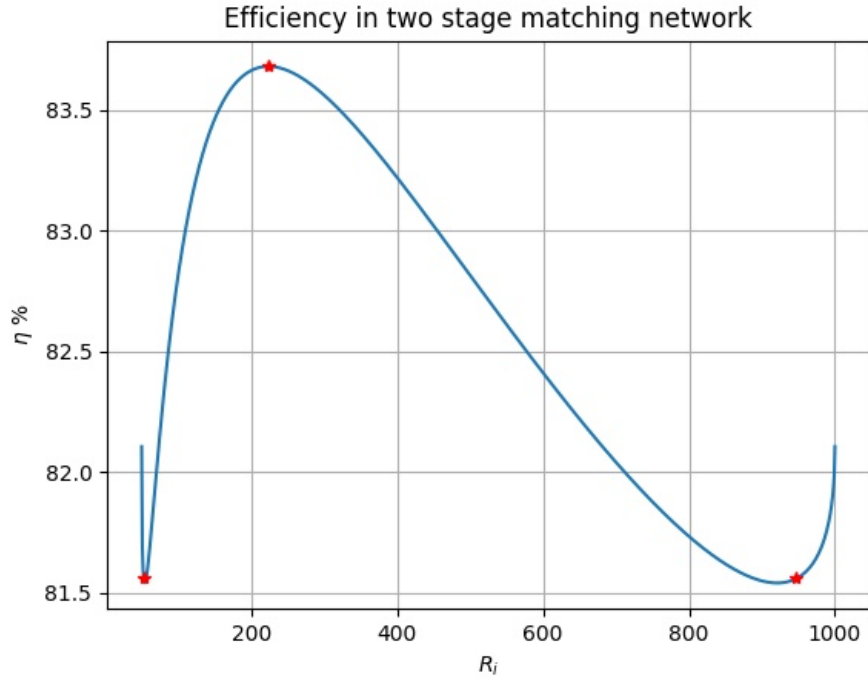
$$\implies R_i = 223.6, 52.7, 947.213 \quad (13)$$



Plugging in these values in the equation (3) we get highest value for  $R=223.6$

$$\Rightarrow R_i = 223.6 \quad (14)$$

$$\Rightarrow Q_1 = 1.863, Q_2 = 1.863 \quad (15)$$

From equation (5) we get,

$$\eta = 83.69\% \quad (16)$$

From equation (1) and (2) we get,

$$L_1 = Q_1 \frac{R_i + \omega L_1 / Q}{\omega} \quad (17)$$

$$\Rightarrow L_1 = \frac{R_i}{\omega(1/Q_1 - 1/Q)} \quad (18)$$

$$L_1 = 73.1nH \quad (19)$$

$$L_2 = \frac{R_{LO}}{\omega(1/Q_2 - 1/Q)} \quad (20)$$

$$L_2 = 16.35nH \quad (21)$$

$$C_1 = \frac{Q_1}{\omega R_{HI}} \quad (22)$$


$$C_1 = 0.29fF \quad (23)$$

$$C_2 = \frac{Q_2}{\omega R_i} \quad (24)$$

$$C_2 = 1.3fF \quad (25)$$

## Problem 2

(a)

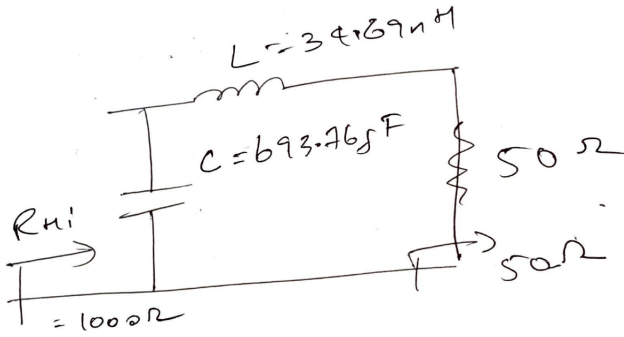

$$R_{HI} = 1000\Omega, R_{LO} = 50\Omega; \omega = 2\pi 10^9$$

$$Q = \sqrt{\frac{1000}{50} - 1} \Rightarrow Q = 4.359 \quad (26)$$


$$Q = \frac{\omega L}{R_{LO}} \Rightarrow L = 34.69nH \quad (27)$$

$$Q = \omega C R_{HI} \Rightarrow C = 693.76fF \quad (28)$$

(b)

Given  $Q_{loaded} = 5$  which means  $Q$  of network is 10.

(i) Low-pass  $\Pi$

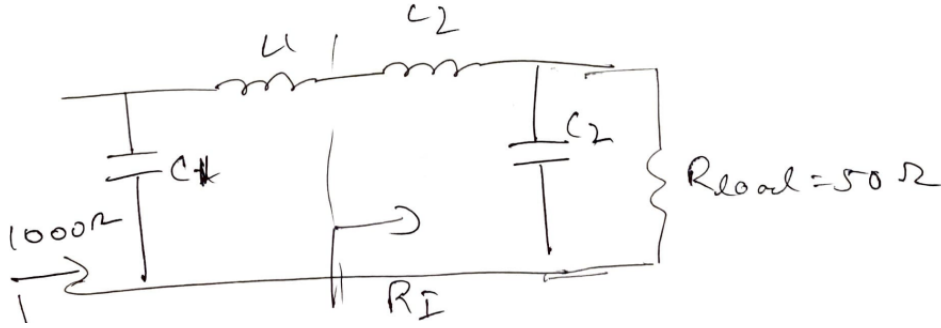


$$Q_1 = \sqrt{\frac{1000}{R_I} - 1} \quad (29)$$

$$Q_2 = \sqrt{\frac{50}{R_I} - 1} \quad (30)$$

$$Q = \sqrt{\frac{1000}{R_I} - 1} + \sqrt{\frac{50}{R_I} - 1} = 10 \quad (31)$$

$$\Rightarrow 104R_I^2 - 2100R_I + 9025 = 0 \Rightarrow R_I = 13.99\Omega \quad (32)$$

(i) Low-pass T

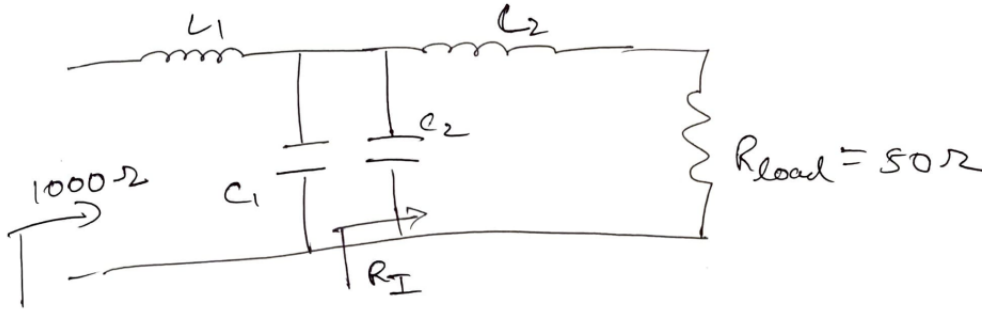

$$Q_1 = \sqrt{\frac{R_I}{R_{HI}} - 1} \quad (33)$$

$$Q_2 = \sqrt{\frac{R_I}{R_{LO}} - 1} \quad (34)$$

$$Q = \sqrt{\frac{R_I}{1000} - 1} + \sqrt{\frac{R_I}{50} - 1} = 10 \quad (35)$$

$$\Rightarrow R_I^2(3.61e - 4) - 4.2R_I + 10400 = 0 \quad (36)$$

$$R_I = 3574.26\Omega \quad (37)$$