


# ADCs for Direct RF Sampling

Tadipatri Uday Kiran Reddy - EE19BTECH11038


IIT Hyderabad

May 19, 2022

# Introduction

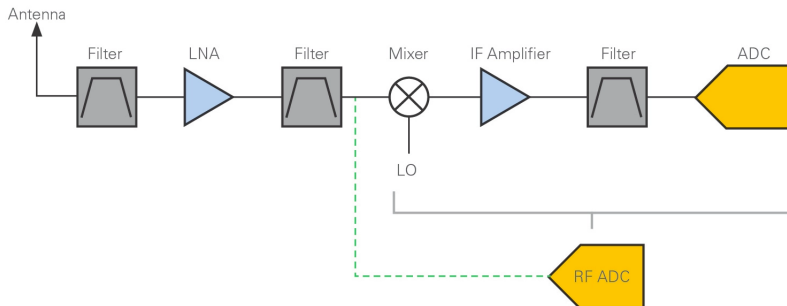


# Introduction

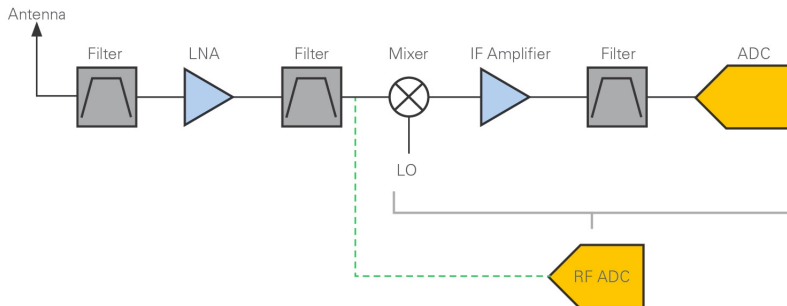


- ADC architecture for sampling at RF with low power and area.

# Introduction

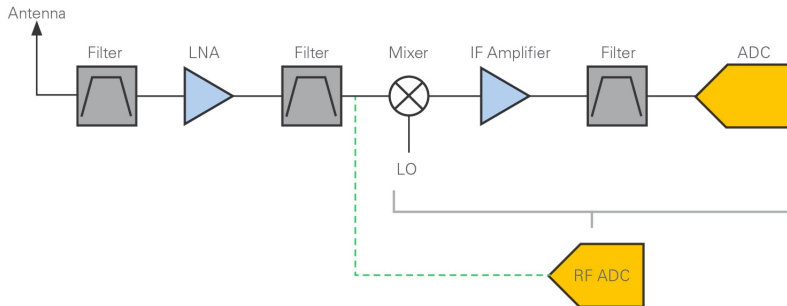


- ADC architecture for sampling at RF with low power and area.
- High sampling rate with relatively slow circuits, *Time-Interleaved ADC*.

# Introduction

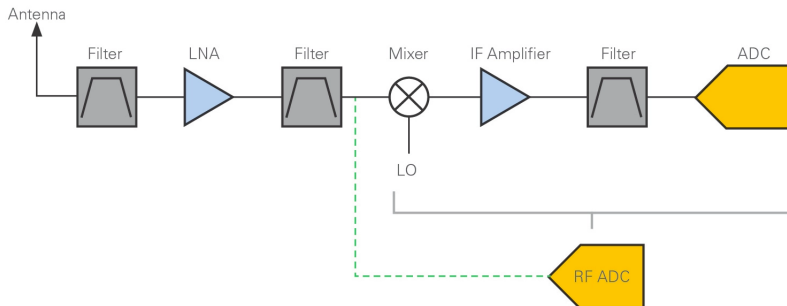


- ADC architecture for sampling at RF with low power and area.
- High sampling rate with relatively slow circuits, *Time-Interleaved ADC*.
- Minimize quantisation and noise error.

# Motivation for RF sampling

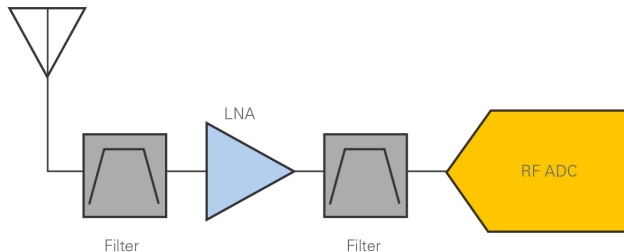

- Simpler hardware design due to elimination of analog frequency conversion.

# Motivation for RF sampling

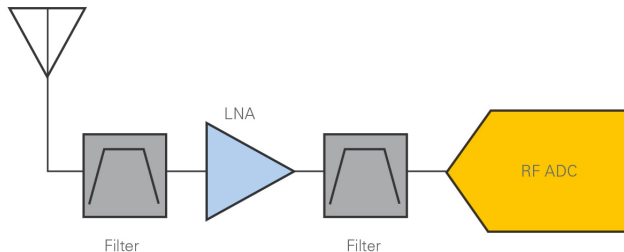

- Simpler hardware design due to elimination of analog frequency conversion.
- Exploit the computing power of DSPs.

# Analog-to-Digital Converters

- Sample the input signal at reconstructable rate and then Quantize.



# Analog-to-Digital Converters

- Sample the input signal at reconstructable rate and then Quantize.

Types of converters,

# Analog-to-Digital Converters

- Sample the input signal at reconstructable rate and then Quantize.

Types of converters,

# Analog-to-Digital Converters

- Sample the input signal at reconstructable rate and then Quantize.

Types of converters,

- Nyquist-rate Converters, double the input bandwidth.

$$SQNR = 6.02ENOB + 1.76dB$$

# Analog-to-Digital Converters

- Sample the input signal at reconstructable rate and then Quantize.

Types of converters,

- Nyquist-rate Converters, double the input bandwidth.

$$SQNR = 6.02ENOB + 1.76dB$$

Noise spectral density is constant!

# Analog-to-Digital Converters

- Sample the input signal at reconstructable rate and then Quantize.

Types of converters,

- Nyquist-rate Converters, double the input bandwidth.

$$SQNR = 6.02ENOB + 1.76dB$$

Noise spectral density is constant!

- Oversampled Converters, very high sampling rate,  $OSR = \frac{f_s}{2f_B}$

$$SQNR = 6.02ENOB + 1.76 + 10\log(OSR)dB$$

# Analog-to-Digital Converters

- Sample the input signal at reconstructable rate and then Quantize.

Types of converters,

- Nyquist-rate Converters, double the input bandwidth.

$$SQNR = 6.02ENOB + 1.76dB$$


Noise spectral density is constant!

- Oversampled Converters, very high sampling rate,  $OSR = \frac{f_s}{2f_B}$


$$SQNR = 6.02ENOB + 1.76 + 10\log(OSR)dB$$

Noise spectral density at ROI is less!!

# Limitations of S/H Circuit

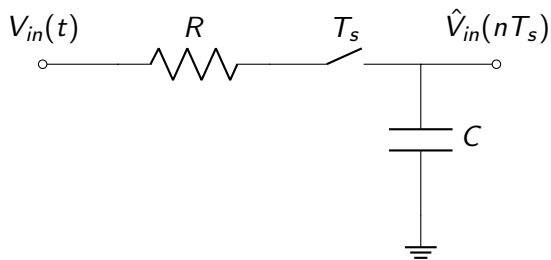


# Limitations of S/H Circuit

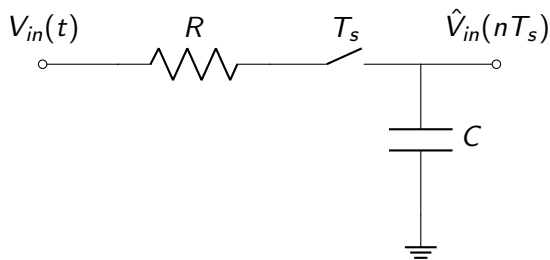

$$\frac{1}{RC} \gg f_{in}$$




## Limitations of S/H Circuit

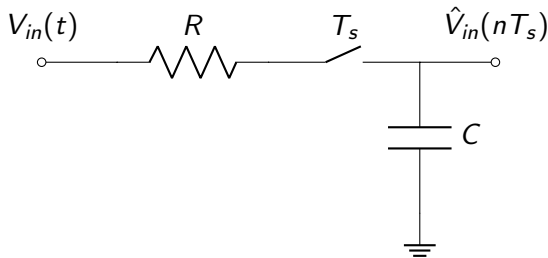

$$\frac{1}{RC} \gg f_{in}$$

- Difficult to construct S/H circuit with very high tracking BW.


## Limitations of S/H Circuit

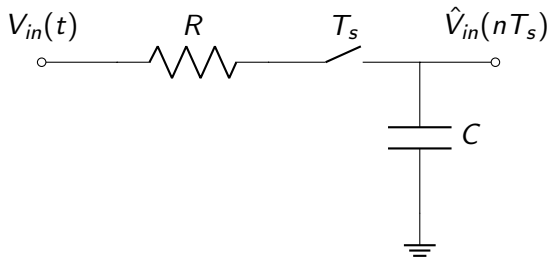


$$\frac{1}{RC} \gg f_{in}$$

- Difficult to construct S/H circuit with very high tracking BW.
- Due to Low pass nature RF signal will attenuate.

# Time-Interleaved ADC

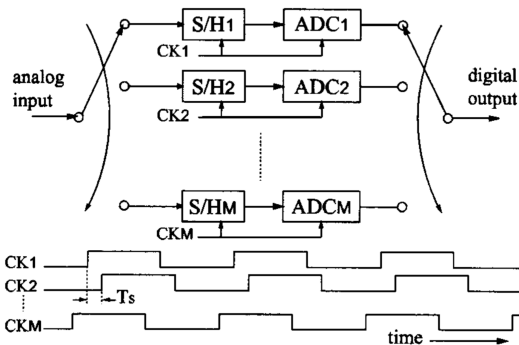


# Time-Interleaved ADC

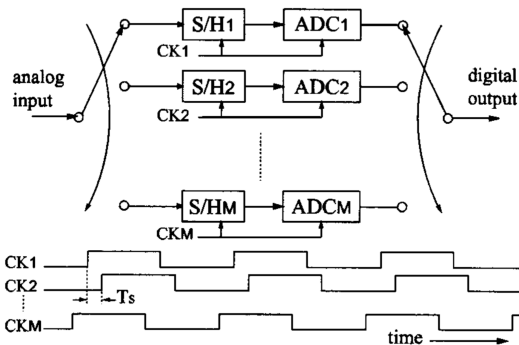


- Required clock,  $f_{clk} = f_s / M$

# Time-Interleaved ADC

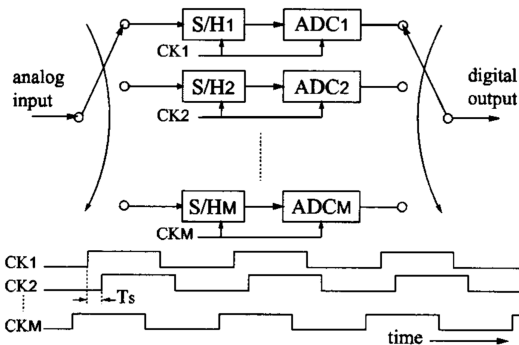


- Required clock,  $f_{clk} = f_s/M$
- Phase difference,  $\phi_i = \frac{2\pi(i-1)}{M}$

# Analysis of ADC based on VCO

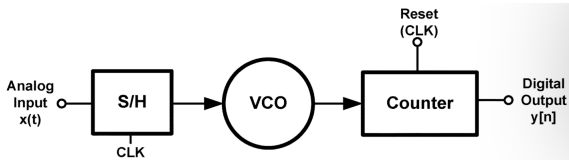


# Analysis of ADC based on VCO

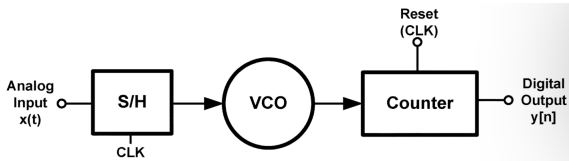

- VCO translates the input voltage to phase.

# Analysis of ADC based on VCO

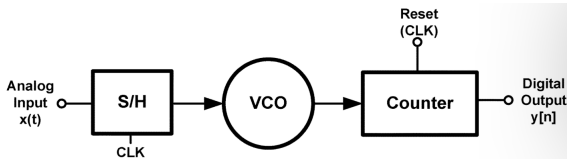


- VCO translates the input voltage to phase.
- Counter, counts the number of rising/falling edges.


$$\phi[n] = \int_{nT_s}^{(n+1)T_s} K_v x[n] dt + p_i[n] = G_v x[n] + e[n-1]$$



# Analysis of ADC based on VCO

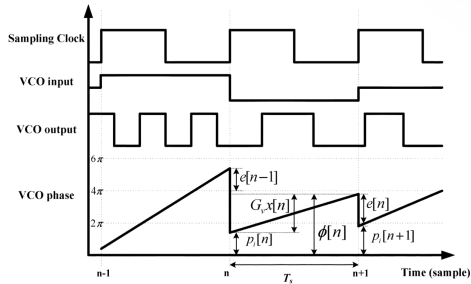

# Analysis of ADC based on VCO

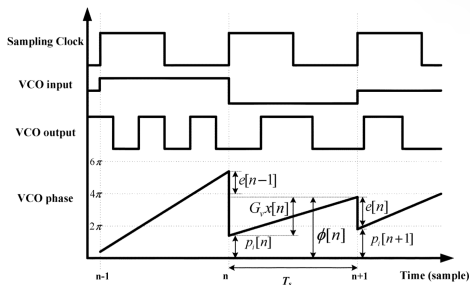


$$y[n] = \frac{1}{2\pi}(\phi[n] - e[n]) = \frac{1}{2\pi}(G_v x[n] + e[n-1] - e[n])$$

$$Y(z) = \frac{1}{2\pi}(G_v X(z) + (z^{-1} - 1)E(z))$$

$$NTF(z) = \frac{1}{2\pi}(z^{-1} - 1) \implies |NTF(e^{j\omega})| = |2\sin(\omega/2)|$$

# Analysis of ADC based on VCO

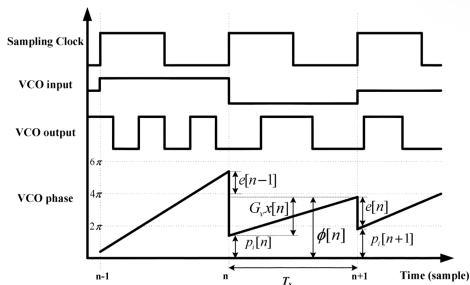

$$y[n] = \frac{1}{2\pi}(\phi[n] - e[n]) = \frac{1}{2\pi}(G_v x[n] + e[n-1] - e[n])$$

$$Y(z) = \frac{1}{2\pi}(G_v X(z) + (z^{-1} - 1)E(z))$$

$$NTF(z) = \frac{1}{2\pi}(z^{-1} - 1) \implies |NTF(e^{j\omega})| = |2\sin(\omega/2)|$$

- First order high-pass filter.

## Extension for N-th order ADC

$$NTF(z) = \frac{1}{2\pi}(z^{-N} - 1)$$

## Extension for N-th order ADC

$$NTF(z) = \frac{1}{2\pi}(z^{-N} - 1)$$

- Zeros will occur when  $z = 1^{1/N} \implies \omega_k = \frac{2\pi(k-1)}{N}$ .

## Extension for N-th order ADC


$$NTF(z) = \frac{1}{2\pi}(z^{-N} - 1)$$

- Zeros will occur when  $z = 1^{1/N} \implies \omega_k = \frac{2\pi(k-1)}{N}$ .
- We will try to center our signal frequency at these zeros.

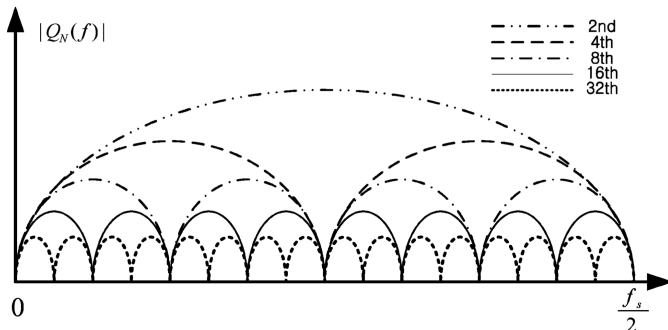
## Extension for N-th order ADC

$$NTF(z) = \frac{1}{2\pi}(z^{-N} - 1)$$

- Zeros will occur when  $z = 1^{1/N} \implies \omega_k = \frac{2\pi(k-1)}{N}$ .
- We will try to center our signal frequency at these zeros.



## Which Zero to center at?

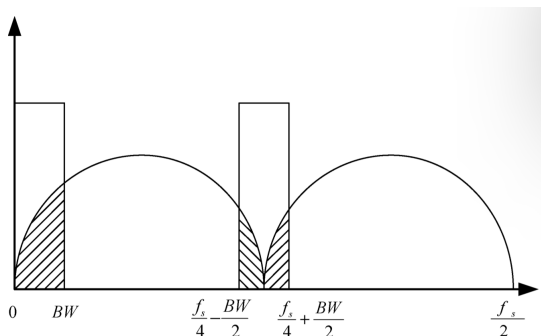

- At  $\omega = 0$  or  $\pi$ ,

$$SQNR = 6.02ENOB - 3.41 + 30\log(OSR)dB$$

- At intermediate zeroes,

$$SQNR = 6.02ENOB - 3.41 + 6.02 + 30\log(OSR)dB$$


Increase of 6.02dB is equivalent to increase in 1-bit precision of ADC!!





# Non-idealities

- DC offset
- Gain mismatch
- Clock Jitter/Skew
- Bandwidth mismatch
- Non-linearity in VCO



# DC offset

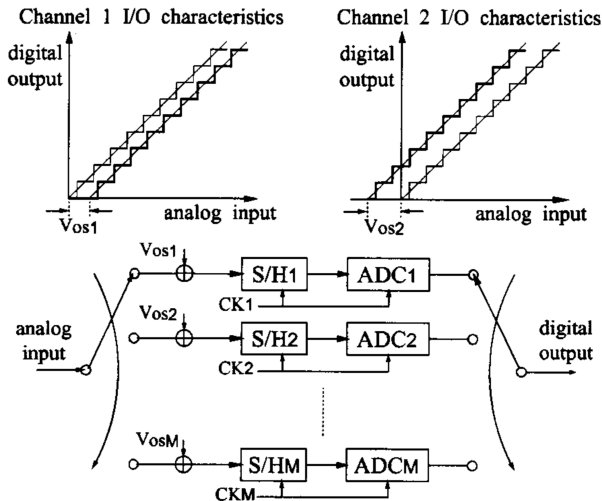

# DC offset

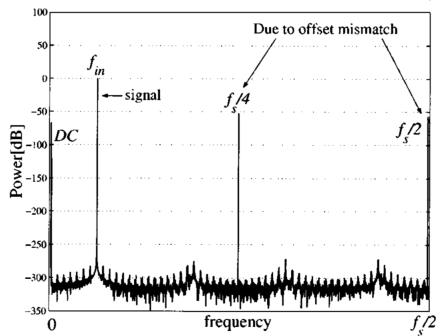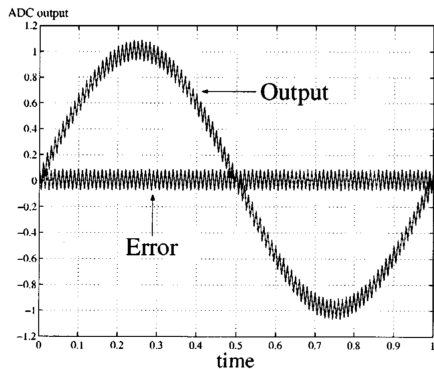


# DC offset

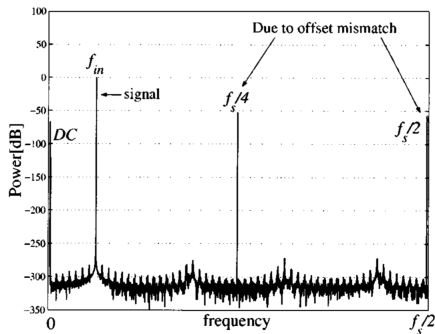
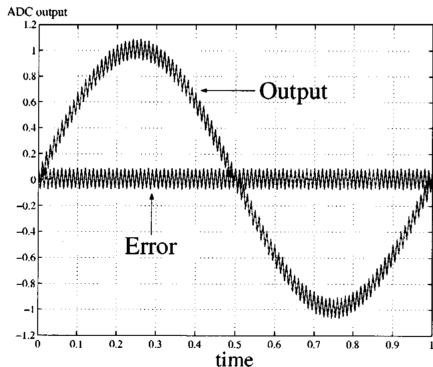


- We can see that dc offset periodicity  $\Rightarrow$  peaks at  $\frac{k}{M} f_s$



# Gain mismatch

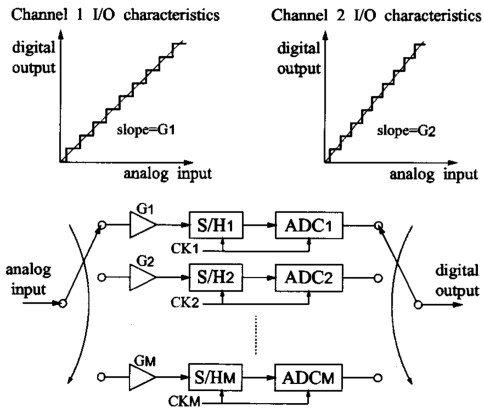

# Gain mismatch

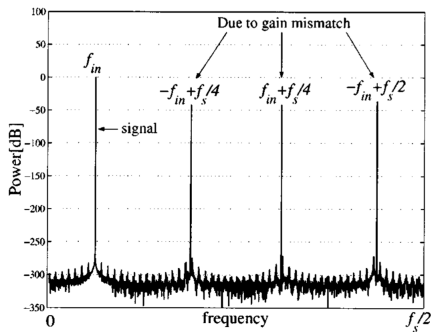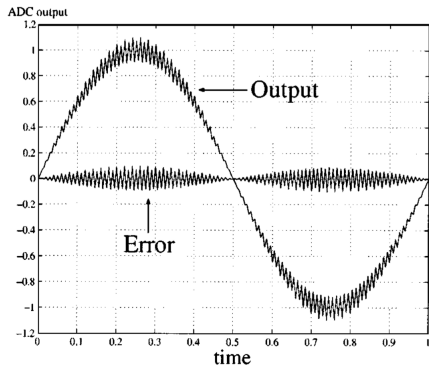


# Gain mismatch

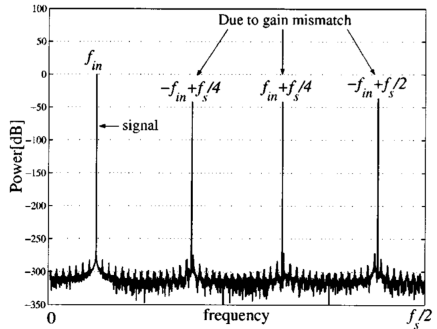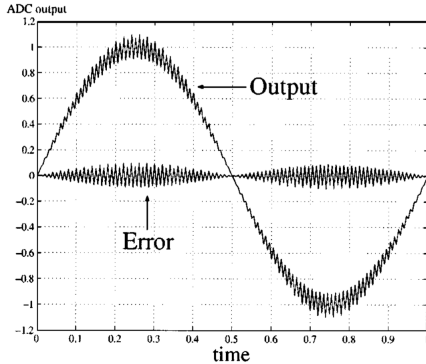



- Gain mismatch can be looked as A.M  $\Rightarrow$  peaks at  $\pm f_{in} + \frac{k}{M} f_s$
- Error at higher amplitude is more.

# Clock jitter


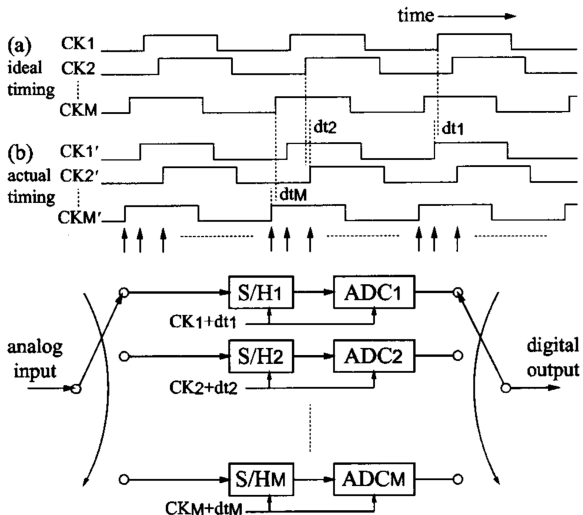




# Clock jitter

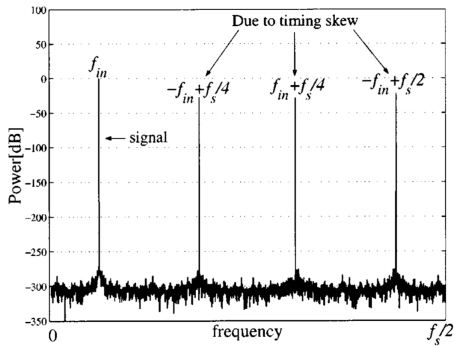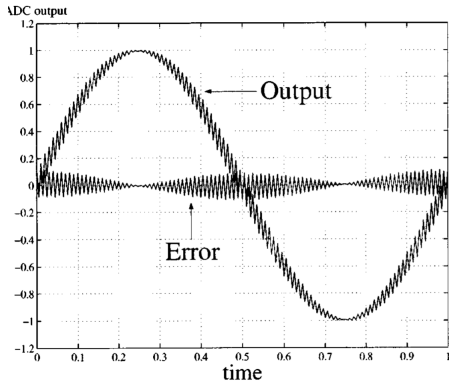


# Clock jitter

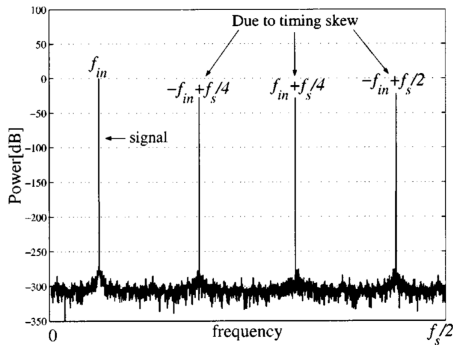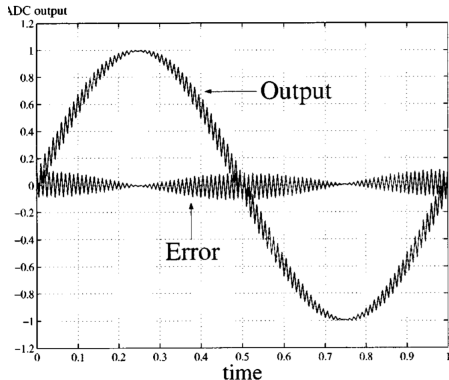

- Clock skew behaves like P.M  $\implies$  peaks at  $\pm f_{in} + \frac{k}{M} f_s$ .
- Error is high at places where slew rate is more.

# SNR comparisons

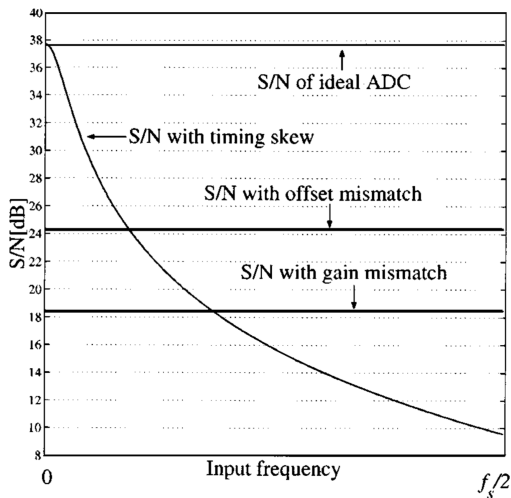

# Thank You