
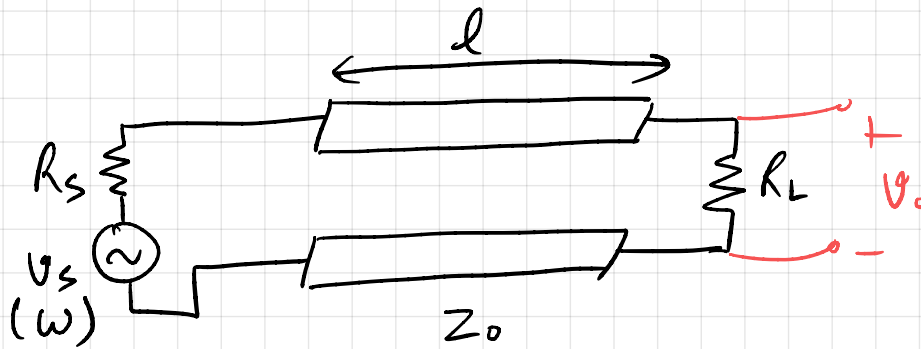


①

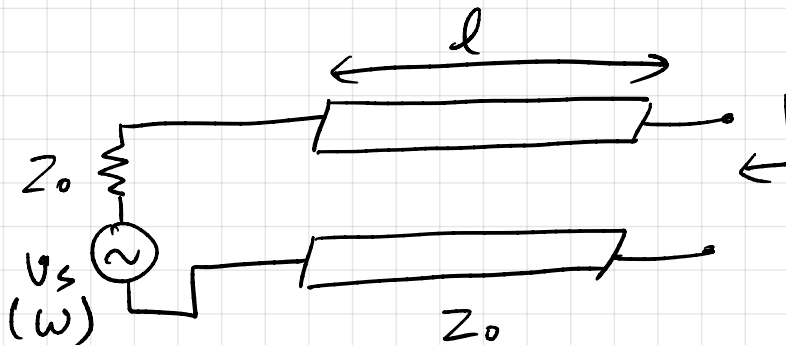


Find V_o in the above network.

②



Find Thevenin equivalent of the above network.

③

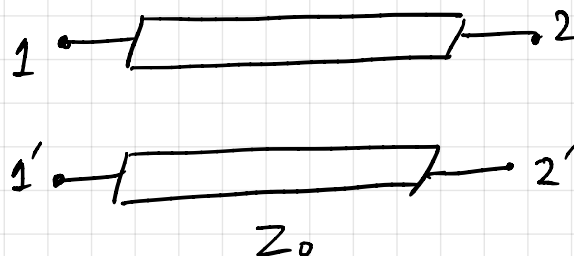

Find delay of the above lossless T.L. if its total capacitance is C_T .