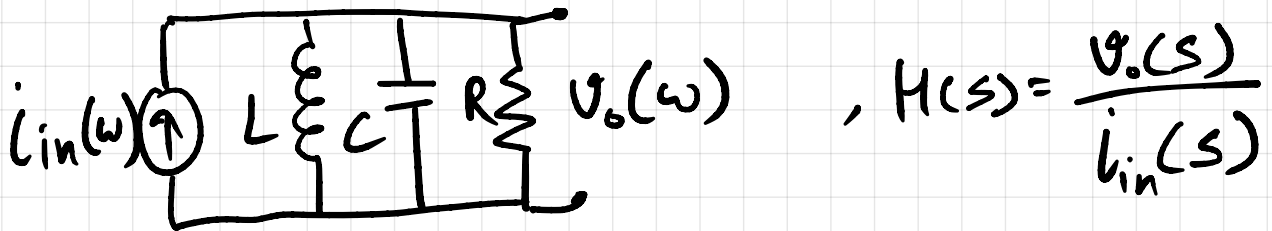



Assignment1  
EE5192 2022  
akumar@ee.iith.ac.in

1. Dual of a series RLC filter is a parallel RLC network as shown below:



Find the transfer function  $H(s)$ ,  $Q$  of the network and 3dB bandwidth.

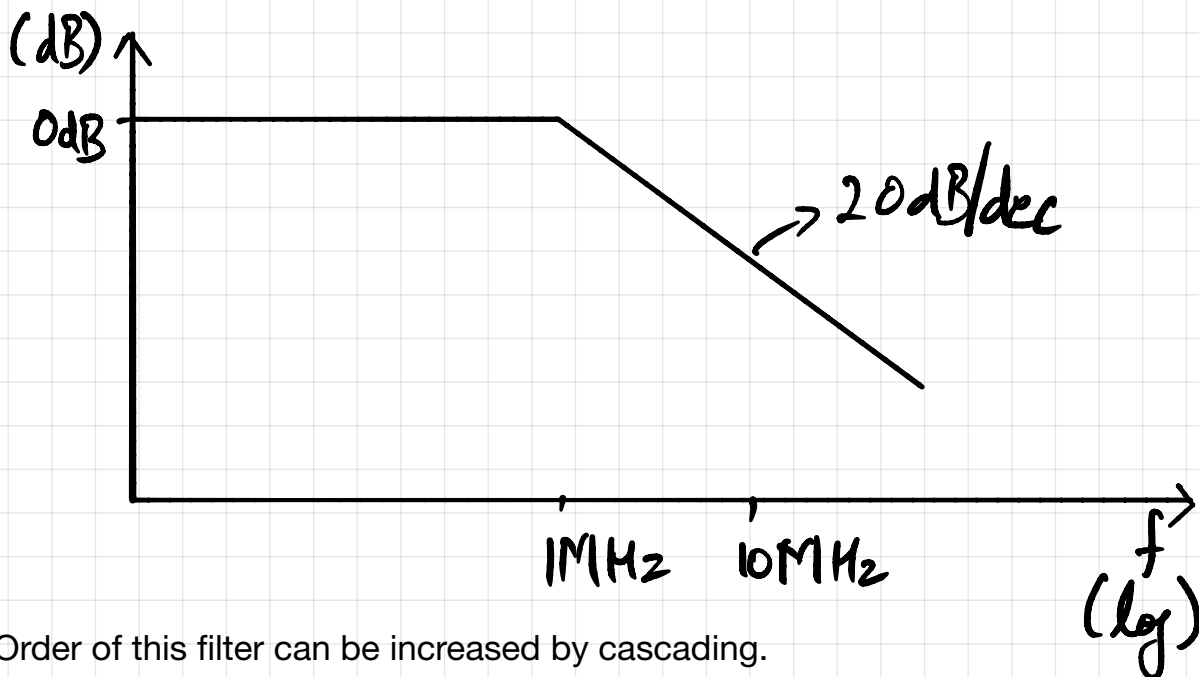2. Below is an approximate frequency response of a first order low-pass filter:




Order of this filter can be increased by cascading.

(a) What should be the order such that when roll-off starts at  $1MHz$ ,  $40dB$  attenuation is achieved at  $10MHz$ ?


(b) Find the order when filter roll-off starts at  $100MHz$  and  $40dB$  attenuation is required at  $109MHz$ .

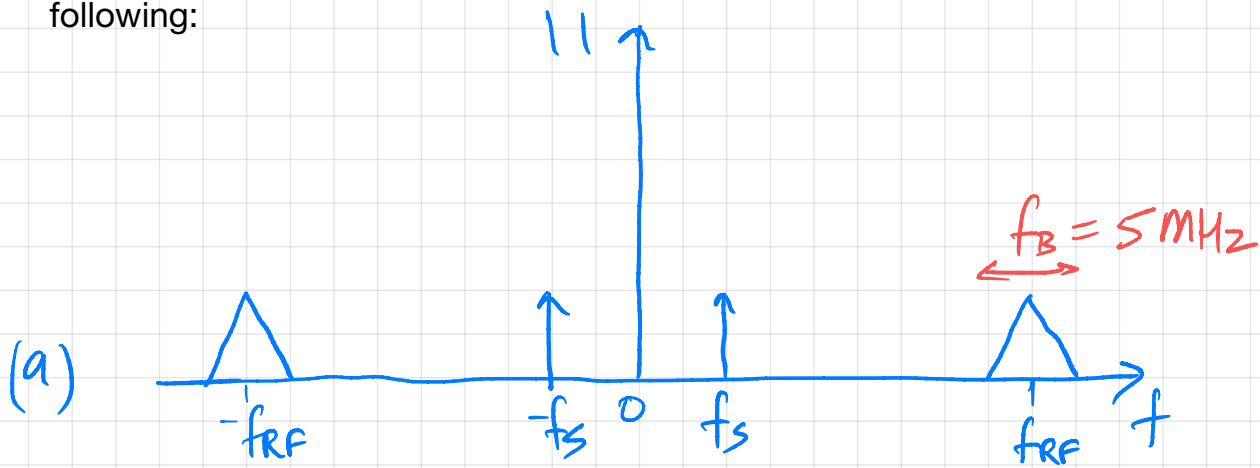3. Draw the spectrum of sampled output showing at least three alias bands for the following:



Case I  $\rightarrow f_s = 5 \text{ MHz}, f_{RF} = 1 \text{ GHz}$

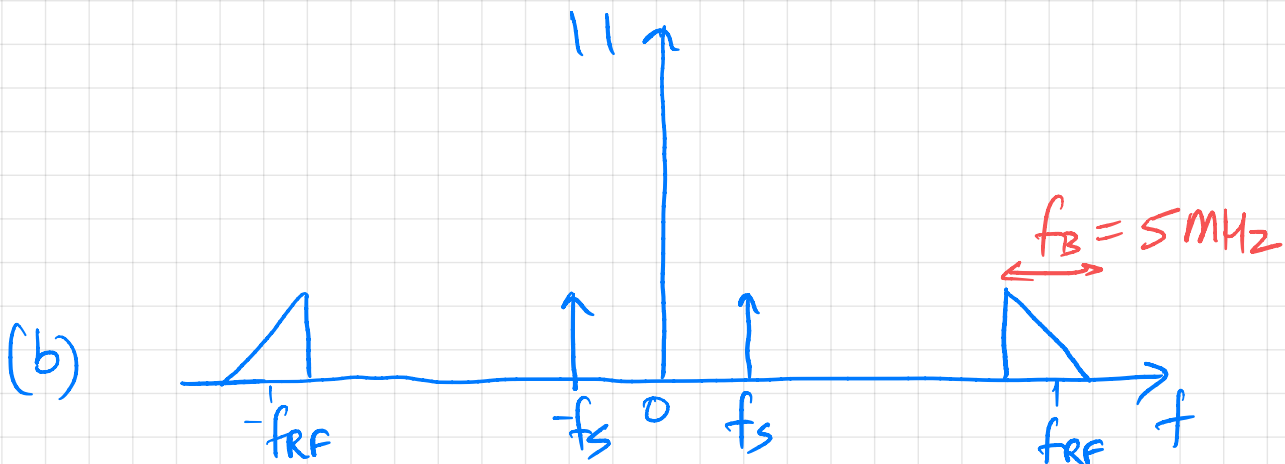Case II  $\rightarrow f_s = 5 \text{ MHz}, f_{RF} = 1 \text{ GHz} + 3 \text{ MHz}$



Case I  $\rightarrow f_s = 5 \text{ MHz}, f_{RF} = 1 \text{ GHz}$

Case II  $\rightarrow f_s = 5 \text{ MHz}, f_{RF} = 1 \text{ GHz} + 3 \text{ MHz}$

What is the minimum  $f_s$  to avoid signal corruption in all the above cases?

4. Below is the frequency details of an RF band:

Centre frequency =  $1 \text{ GHz}$ , span =  $100 \text{ MHz}$ , channel bandwidth =  $10 \text{ MHz}$ .

Channel select filter is chosen to operate at  $300 \text{ MHz}$  with  $10 \text{ MHz}$  bandwidth.

(a) Find the range of LO frequency to cover the entire band.

(b) Find the centre frequency and span of image.